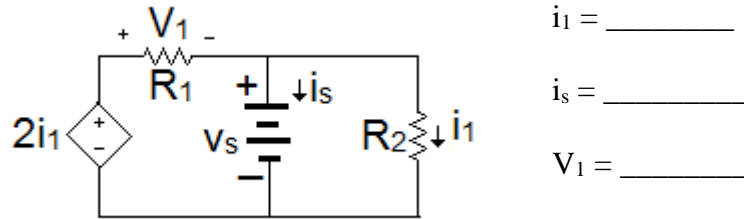



EE 210
Hour Exam 1

Name _____
 September 10, 2015


1. In the circuit below $R_1 = R_2 = 1\Omega$ and $V_s = 3$ volts. Find the value of i_1 , i_s , and V_1 in the circuit below. Show all of your work.



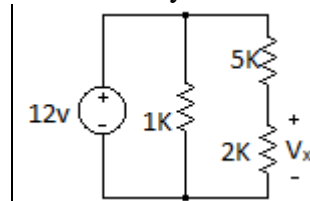
2. Use voltage division to find the value of V_x in the circuit below. Show your work.



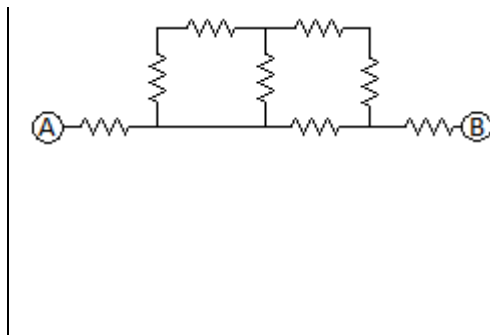
3. All of the resistors in the following circuit have a value of 1Ω . Find the value of the resistance between points A and B.



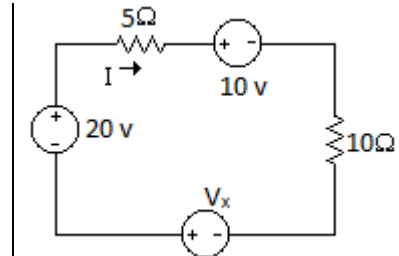
4. For the circuit below the value of I is 0.25 amps. Find the value of V_x .



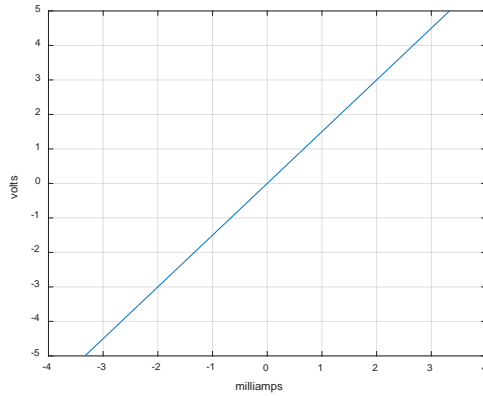
5. The graph below is a plot of voltage vs current for a resistor. What is the value of the resistance? Show your work



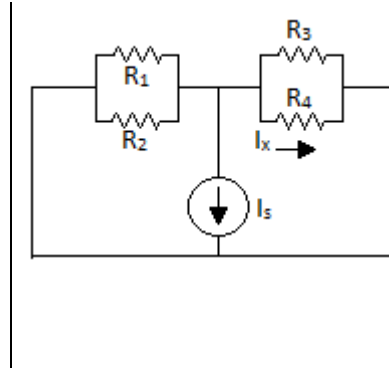6. In the circuit below $I_s = 10 \text{ ma}$, $R_1 = 1\text{K}$, $R_2 = 4\text{K}$, $R_3 = 2\text{K}$, and $R_4 = 8\text{K}$. Find I_x .



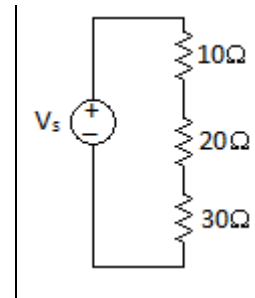7. The power dissipated by the 10Ω resistor is 5 watts. Find V_s .



8. Find i_0 in the following circuit.

