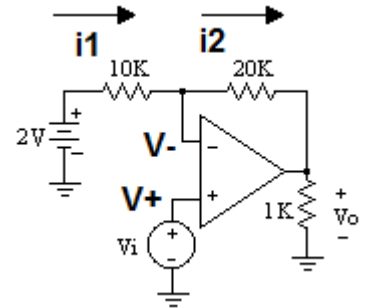



1. In the circuit below $V_i = 3$ volts. What is the value of V_o . Show all work.




2. For each circuit below determine the output voltage V_o if $V_i = 3$ volts.

<p>A)</p>	<p>B)</p>	<p>C)</p>
<p>$V_o =$ _____</p>	<p>$V_o =$ _____</p>	<p>$V_o =$ _____</p>

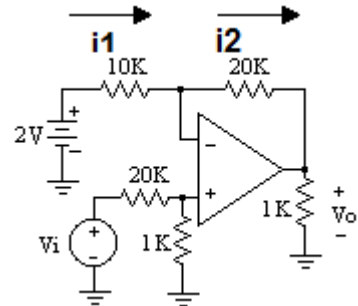3. In the circuit below $V_i = 30$ volts. What is the value of V_o . Show all work.



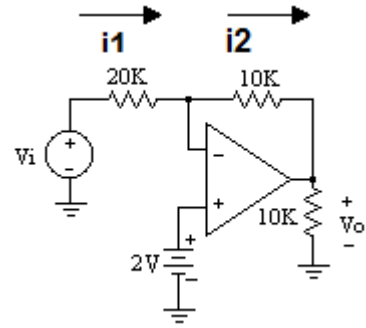4. In the op-amp circuit below $V_i = 4$ volts. What is the value of V_o . Show all work.



5. Answer the questions below about the op amp circuit shown. Take the input voltage V_i to be 0.4 volts

- A) Will the output voltage be positive or negative?
- B) What will be the voltage at node A?
- C) What will be the voltage at node B?
- D) What is the output voltage.

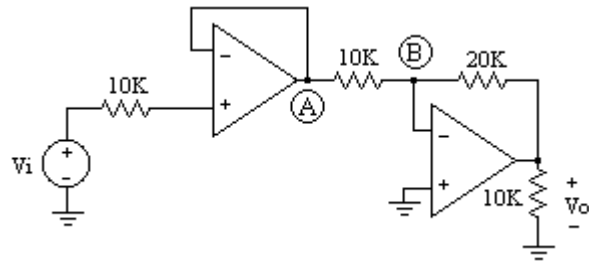


Figure 5
Circuit for problem 5.

6. Find the relationship between V_o and V_i for the op amp circuit in Figure 6.



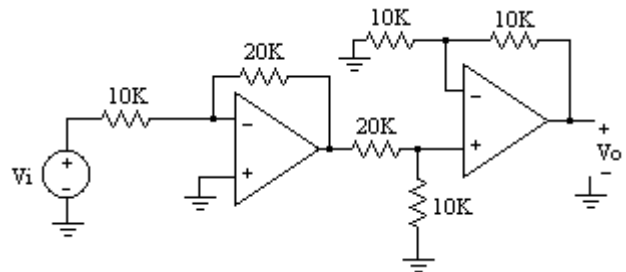


Figure 6
Op amp circuit for Problem 6

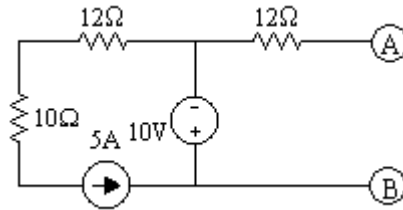7. Find the Thevenin equivalent circuit at A-B



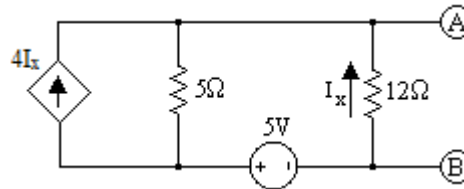8. Find the value of the current I_x in the circuit below. Show all work.



9. Draw a circle around all of those equations listed below which correctly apply to the circuit shown in Figure 1.

A) $2I_1 + (I_1 - I_2) = -22$

B) $(I_2 - I_1) + 4I_2 = 14$

C) $2V_A - 40 + 4V_A + 8 + V_A + 16 = 0$

D) $2I_1 + 4I_2 = -36$

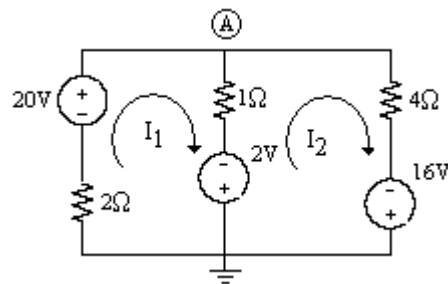


Figure 1
Circuit for problem 1

10. Answer the questions below about the circuit shown.

A) Write the mesh equation for I_1 .

B) Find the value of V_x

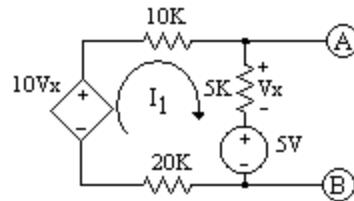


Figure 4
Circuit for problem 4

C) Find the open circuit voltage at A-B

D) Find the short circuit current at A-B

E) Draw the Thevenin equivalent circuit.

11. Find the Thevenin equivalent circuit for the circuit shown in Figure 3. Show all work.

