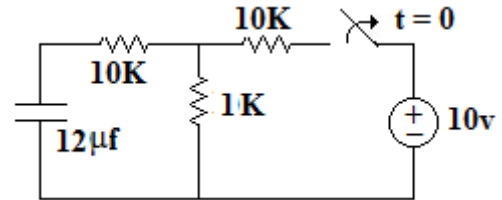


EE 210
MATLAB® Plots

1. Use MATLAB® to plot the voltage vs. time function for the capacitor voltage in the circuit below for $t > 0$.

SOLUTION:


For $t < 0$ the switch is closed and the capacitor can be treated as an open circuit since the voltage has stabilized and there are no transients from $-\infty$ to 0. The capacitor voltage at $t = 0^-$ can be found from the voltage divider.



$$v_c(0^-) = 10 \frac{1}{1+10} = 0.9091 \text{ volts}$$

Because capacitor voltage cannot change instantaneously we have $v_c(0^+) = v_c(0^-) = 0.9091$ volts. For $t > 0$ the switch opens and the circuit becomes that shown below.

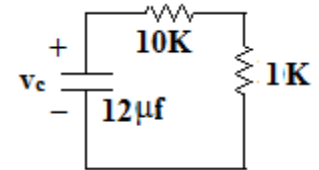If we take the loop current to be i_1 we can write:



$$v_c - i_1 10 - i_1 1 = 0$$

But $i_1 = -C \frac{dv_c}{dt}$ which gives

$$v_c - 11000C \frac{dv_c}{dt} = 0$$

Rearranging and letting $\tau = 11000 \times C = 0.132$

$$\frac{dv_c}{v_c} = -dt / (11000C) = -t / \tau$$

Integrate both sides to get

$$\ln(v_c) = -t / \tau + \ln(k) \text{ where } \ln(k) \text{ is the constant of integration.}$$

This equation can be written as

$$\ln(v_c / k) = -t / \tau \text{ or}$$

$$v_c = k e^{-t/\tau}$$

When $t = 0^+$ we know that $v_c = 0.9091$ volts. This gives $0.9091 = k$.

Putting in the value of C we get

$$v_c = 0.9091 e^{-t/0.132}$$

In this equation τ is the time constant and is equal to 132 msec. From our experience with time constants we know that the circuit will reach 99% of its final value in about five time constants or about 650 msec. We can use MATLAB® to plot the equation over this time range.

```
%PlotExmpl.m
tau = .132;
%t goes from 0 to 1 msec in steps of 1 usec
t = 0:.01:1;
%this is the expression for vc
vc = 0.9091*exp(-t/tau);
figure(1);clf;           %Create a figure
plot(t, vc);            %Do the plot
xlabel('time in seconds'); %label x axis
ylabel('voltage');      %label y axis
title('Example problem'); %Give a title
```

