
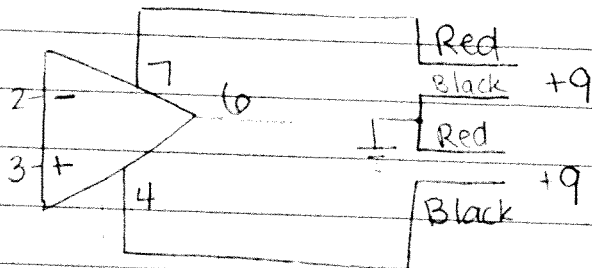


Lab 7: Op Amps


10/3/13

Inverting and non-Inverting Amplifier

LM 741

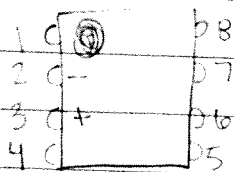

Inverting Amplifier

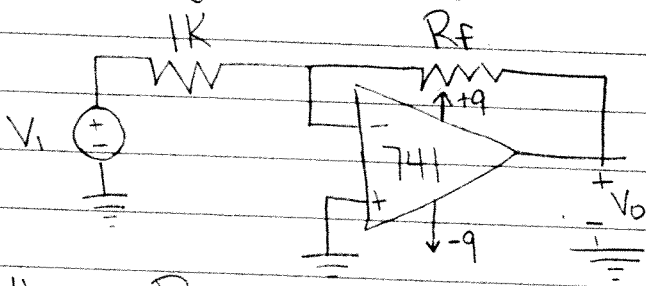

1) When $R_f = 510 \Omega$, we measured:

$$V_o = -2.5$$

$$\frac{V_o}{V_s} = \frac{-2.5}{5} \approx -0.5 \text{ gain}$$

When $R_f = 10k$, we measured:

$V_o = -6.9$, but that is because it is saturated

$$\frac{V_o}{V_s} \approx -50 \text{ gain}$$


When $R_f = 100k$, we measured:


$V_o = -7.02$, but that is because it is saturated

$$\frac{V_o}{V_s} \approx -500 \text{ gain}$$

2) 10/8/13

Ch. 1: 500mv Ch. 2: 500m

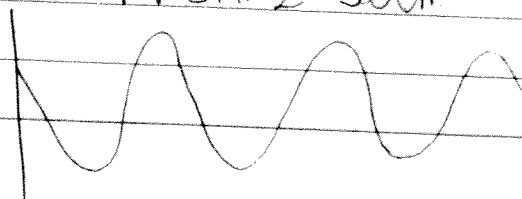

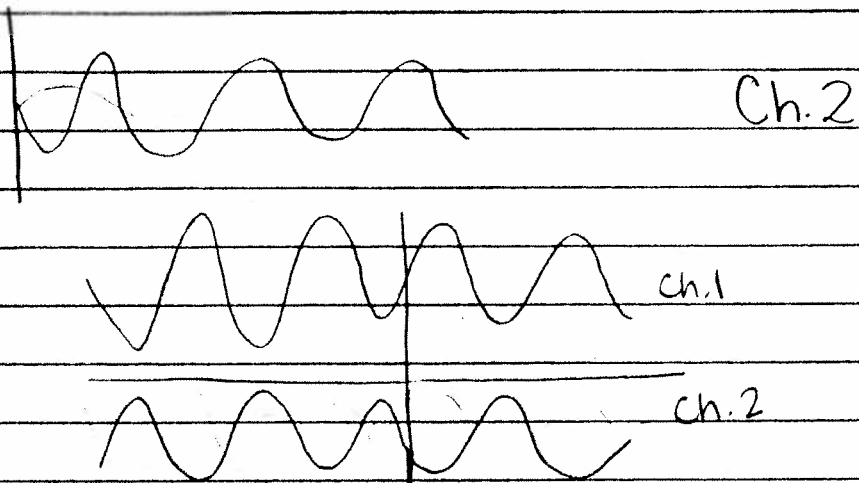

Ch1: Pk-Pk 700mV

Ch1 Mean: -8.82mV

Ch2 Pk-Pk 380mV

Ch. 2 Mean: 7.52mV


Ch 1 Pos. Width 498 μ s

$$\frac{\text{Ch. 2}}{\text{Ch. 1}} = \text{gain}$$

$$\frac{380}{700} = \text{gain}$$

gain = .540 this matches our calculated in part 1

Noninverting amplifier

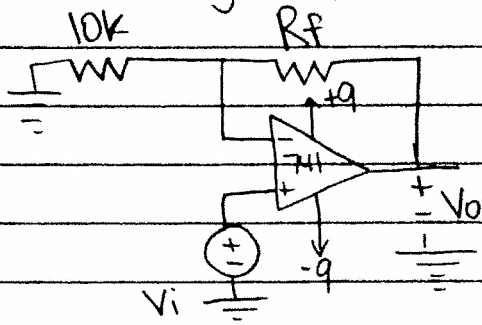

1) When $R_f = 510\Omega$, we measured:

Between inverting and noninverting = .1mV

$$\frac{R_f + 10k}{10k} = \frac{510k + 10k}{10k} = 1.05 \text{ gain}$$

When $R_f = 10k$, we measured:


Between inverting and noninverting = $-0.1mV$
$$\frac{R_f + 10k}{10k} = \frac{10k + 10k}{10k} = 2.00 \text{ gain}$$

When $R_f = 100k$, we measured:

$$\frac{R_f + 10k}{10k} = \frac{100k + 10k}{10k} = 11 \text{ gain}$$

Between inverting and noninverting = $4.24V$,
but this is because it's saturated

2)

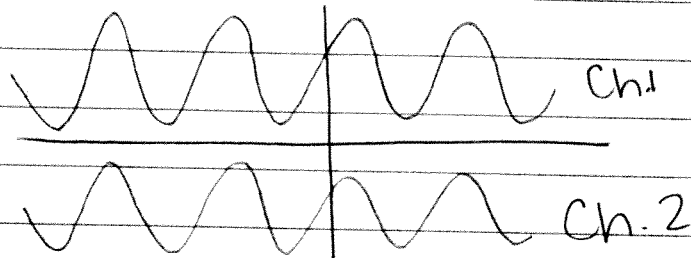

Ch1 Pk-Pk 704mV

Ch1 Mean: $-1.72mV$

Ch.2 Pk-Pk $1.46V = 1460mV$

Ch2 Mean $4.25mV$

$\frac{\text{Ch.2 Pk-Pk}}{\text{Ch1 Pk-Pk}} = \text{gain}$

$$\frac{1460mV}{704mV} = \text{gain}$$

gain = 2.07 this matches our calculated
in part 1 with $R_f = 10k$