

EE 210

Capacitor/Inductor Notes

Capacitors

1. Since $i = Cdv/dt$ when v is not changing (dc) $i = 0$;
2. A capacitor is an open circuit to dc
3. Since $i = Cdv/dt$, if v is discontinuous $i = \infty$.
4. In general, you cannot change the capacitor voltage instantaneously.
5. The ideal capacitor does not dissipate energy. It accepts charge, stores it, and returns it to the circuit.
6. A real capacitor can be modeled as an ideal capacitor in parallel with a large resistor. The resistance may be $100\text{ M}\Omega$ or so.
7. Capacitors in parallel add (like resistors in series).
8. Capacitors in series add as their reciprocals (like resistors in parallel).

Inductors

1. Since $v = Ldi/dt$, if i is not changing (dc) $v = 0$.
2. An inductor looks like a short to dc.
3. If inductor current changes instantaneously $di/dt = \infty = v$.
4. In general, you cannot change inductor current instantaneously.
5. An ideal inductor does not dissipate energy but stores it in a magnetic field.
6. A practical inductor can be modeled as an ideal inductor in series with a small resistor and the resistor/inductor combination is in parallel with a small capacitor.
7. Inductors in parallel add as their reciprocals (like resistors in parallel).
8. Inductors in series add (like resistors in series).