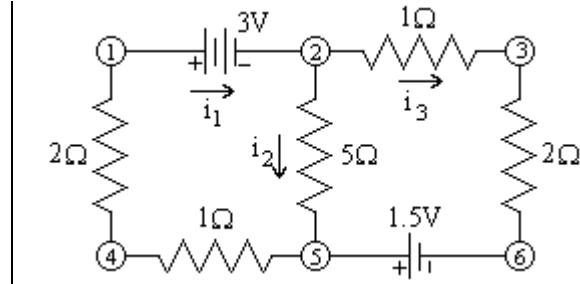



EE 210
Hour Exam 1

Name _____
 September 7, 2017


1. For the circuit below write the equation for the loop around nodes 1, 2, 3, 6, 5, 4 in terms of i_1 , i_2 , i_3 , the battery voltages, and the resistor values.



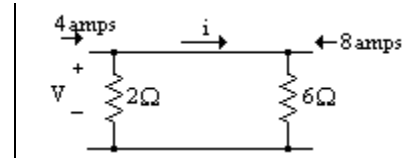
2. In the circuit below find the values of V and i . Show all work.



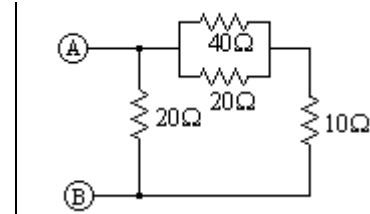
3. For the circuit below find the equivalent resistance at terminals A-B. Show all work.



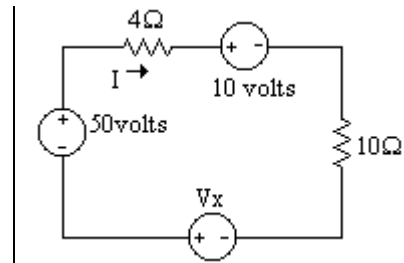
4. For the circuit shown the value of I is known to be 0.40 amps. Find the value of V_x . Show all work.



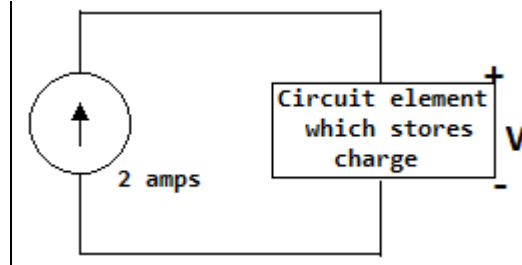
5. Suppose that I have a circuit element which is capable of storing charge. The voltage across the element is proportional to the stored charge. If the proportionality constant is C we can write $q = CV$ where q is the stored charge and V is the voltage across the element. If the circuit element is connected to a constant current source as shown below write the equation for the voltage.



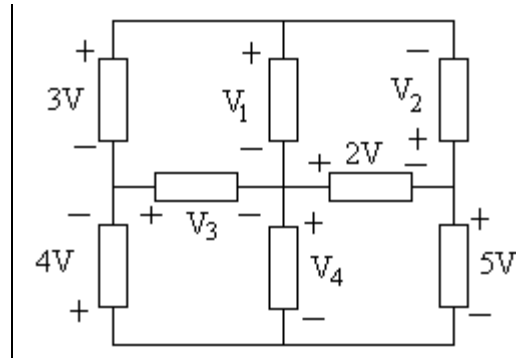6. Each block in the circuit diagram below represents a circuit element. Find the values of V_1 , V_2 , V_3 , and V_4 . Show all work.



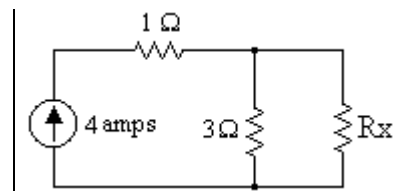
7. In the circuit below find the value of R_x such that the power dissipated by R_x is 12 watts.




8. Find v_1 and i_1 for each of the following:

(a) $v_1 = \underline{\hspace{2cm}}$ $i_1 = \underline{\hspace{2cm}}$

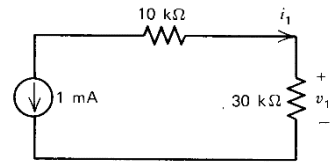(b) $v_1 = \underline{\hspace{2cm}}$ $i_1 = \underline{\hspace{2cm}}$



(b)

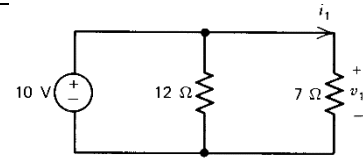

(d)