


## EE 210

### RC Transient Response

In the circuit below the capacitor is uncharged and the switch is in position *a*. At  $t = 0$ , the switch is moved to position *b*. After 15 msec the switch is moved again to position *c*.

A) Find the expression for the voltage across the capacitor for  $t > 0$ .

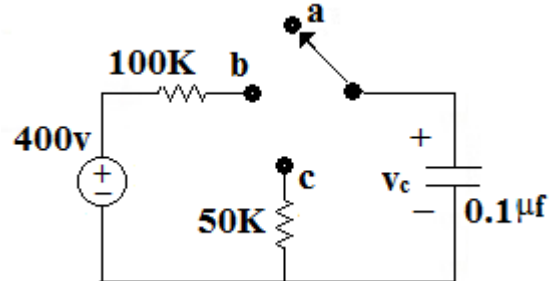B) Use MATLAB® to plot the capacitor voltage vs. time.



Part A)

The capacitor is initially uncharged. At  $t = 0$  the switch moves to position *b*. The initial capacitor voltage is 0 and the final capacitor voltage at  $t = \infty$  will be 400 volts. The solution is of the form

$$v(t) = v_{final} - (v_{init} - v_{final})e^{-t/\tau}$$

In our case  $v_{final} = 400$  volts and  $v_{init} = 0$ . The value of  $\tau$  is  $100 \times 10^3 \times 0.1 \times 10^{-6} = 0.01$ .

This gives

$$v_c(t) = 400(1 - e^{-100t}) \text{ for } t > 0.$$

At  $t = 15$  msec the switch moves to position *c*. The value of the capacitor voltage at 15 msec will be

$$v_c(0.015) = 400(1 - e^{-100 \times 0.015}) = 310.75 \text{ volts}$$

When the switch is moved to position *c*, the initial capacitor voltage will be 310.75 volts. The final capacitor voltage with the switch in position *c* will be 0 volts and the time constant will be  $50 \times 10^3 \times 0.1 \times 10^{-6} = 0.005$  sec

The capacitor voltage is given by

$$v_c(t) = 0 + (310.75 - 0)e^{-200(t-0.015)} \text{ Or } v_c(t) = 310.75e^{-200(t-0.015)}$$

Part B)

```
%RCTransient.m
incr = 0.0001; %tenth of a msec
t1 = 0:incr:0.015; %0 to 15 msec
t2 = 0.015:incr:0.030; %15 to 30 msec
vc1 = 400*(1 - exp(-100*t1));
vc2 = 310.75*exp(-200*(t2 - 0.015));
t = [t1 t2]; %Form a single vector
vc = [vc1 vc2]; %for plotting
figure(1);clf;
plot(t, vc);
xlabel('time in seconds');
ylabel('voltage');
title('RC Circuit response');
```

