

EE 210
Parallel RLC Notes


KCL

$$\frac{v}{R} + \frac{1}{L} \int_{-\infty}^t v dt + C \frac{dv}{dt} = 0$$

or

$$\frac{d^2 v}{dt^2} + \frac{1}{RC} \frac{dv}{dt} + \frac{v}{LC} = 0$$

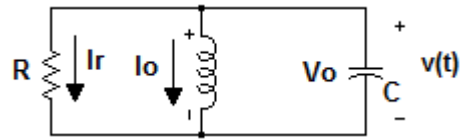This is a second order linear differential equation with constant coefficients



Characteristic equation :

$$s^2 + \frac{1}{RC} s + \frac{1}{LC} = 0$$

Roots are:

$$s_1 = -\frac{1}{2RC} + \sqrt{\left(\frac{1}{2RC}\right)^2 - \frac{1}{LC}} \quad \text{and} \quad s_2 = -\frac{1}{2RC} - \sqrt{\left(\frac{1}{2RC}\right)^2 - \frac{1}{LC}}$$

Let $\alpha = \frac{1}{2RC}$ = Damping factor

$\omega_0 = \frac{1}{\sqrt{LC}}$ = Resonant frequency in radians/sec

Then

$s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$ s_1 and s_2 are called *natural frequencies*

For $\alpha^2 - \omega_0^2 > 0$ the system is *over damped*.

Solution is $i(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$

For $\alpha^2 - \omega_0^2 = 0$ the system is *critically damped*.

Solution is $i(t) = (A_1 + A_2 t) e^{-\alpha t}$

For $\alpha^2 - \omega_0^2 < 0$ the system is *under damped*.

Solution is $i(t) = e^{-\alpha t} [B_1 \cos(\omega_d t) + B_2 \sin(\omega_d t)]$

where $\omega_d = \sqrt{\omega_0^2 - \alpha^2}$