

Series RLC Resonant Circuits:

$$\omega_o = \frac{1}{\sqrt{LC}}$$

$$\omega_2, \omega_1 = \pm \frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}} \quad \text{If } Q \geq 10 \text{ then} \quad \omega_2, \omega_1 \approx \omega_o \pm \frac{B}{2}$$

$$B = \omega_2 - \omega_1 \quad \text{OR} \quad B = \frac{R}{L} \quad \text{OR} \quad B = \frac{\omega_o}{Q}$$

$$Q = \frac{\omega_o * L}{R} \quad \text{OR} \quad Q = \frac{1}{\omega_o * R * C} \quad \text{OR} \quad Q = \frac{\omega_o}{B}$$

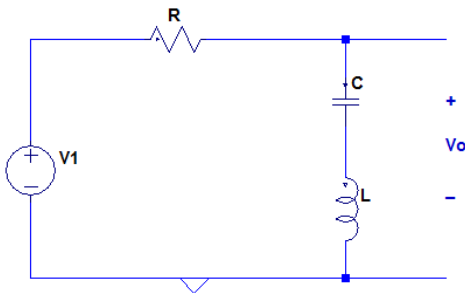


Figure : 1BandStop

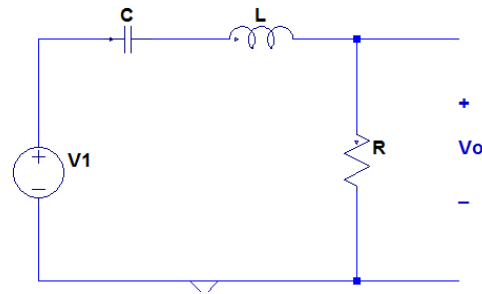


Figure: 2BandPass

Parallel RLC Resonant Circuits:

$$\omega_o = \frac{1}{\sqrt{LC}}$$

$$\omega_2, \omega_1 = \pm \frac{1}{2RC} + \sqrt{\left(\frac{1}{2RC}\right)^2 + \frac{1}{LC}} \quad \text{If } Q \geq 10 \text{ then} \quad \omega_2, \omega_1 \approx \omega_o \pm \frac{B}{2}$$

$$B = \omega_2 - \omega_1 \quad \text{OR} \quad B = \frac{1}{RC} \quad \text{OR} \quad B = \frac{\omega_o}{Q}$$

$$Q = \omega_o RC \quad \text{OR} \quad Q = \frac{R}{\omega_o * L} \quad \text{OR} \quad Q = \frac{\omega_o}{B}$$

